

CHAMP

Chicago side

Eric Oberla

Electronics Godparent Review 10/5/2010

structure

- Full DLL (delay locked loop)
- DLL test structure
- Ring oscillator
- Transmission Lines
- Resistors

Structure/test plans

- Full DLL (delay locked loop)
- DLL test structure -- joint UC/UH eval board
- Ring oscillator (december)
- Transmission Lines – probe pads
- Resistors -- probe pads

DLL

- On-chip, analog DLL will allow us to have a better controlled sampling rate.
- Provide us a cleaner sampling window
- No dead zone of sampling (if the effective delay free running delay line is less than the period of the input clock -> dead time)


 


Figure 1-1 Simplified block diagram of a DLL


DLL - principle

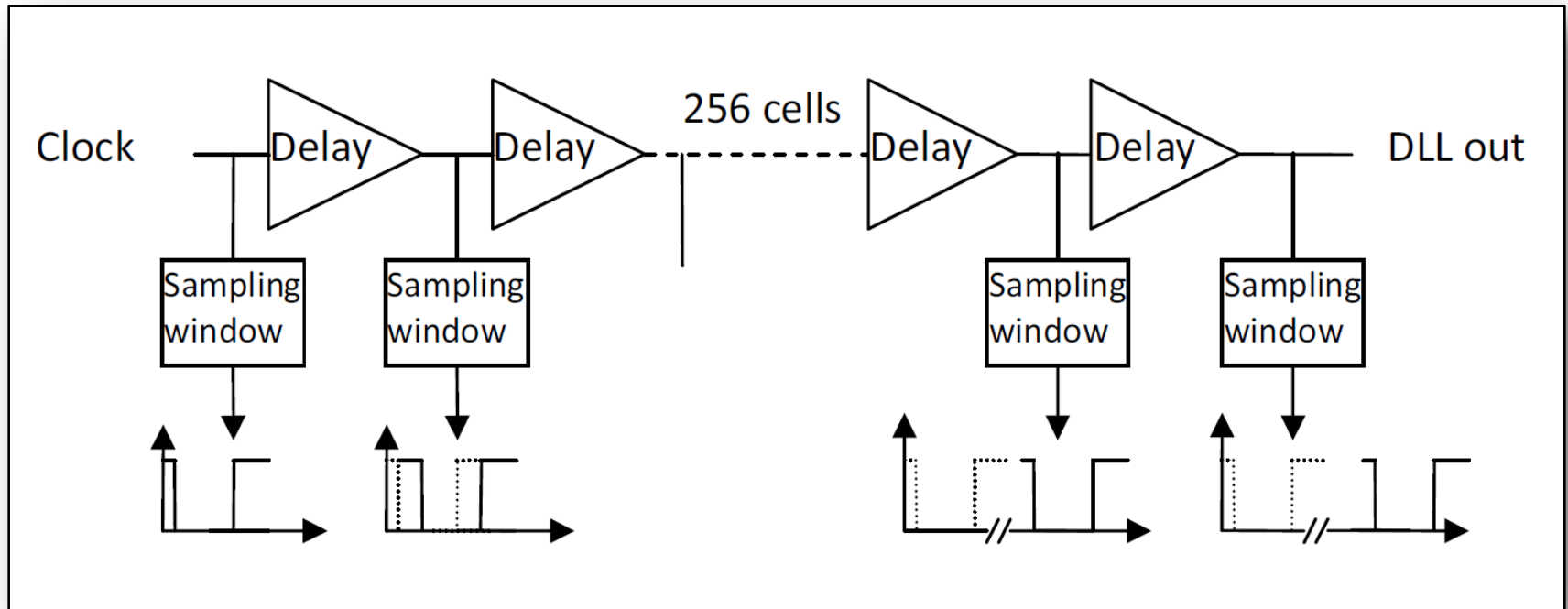- Delay line structure: chain of small delays.



Generates a sampling frequency equal to $\frac{1}{\text{Delay}}$

DLL simulation success

 

summary

- Eval board under development
- Testing in December
- Functional DLL + Hawaii side structures (DACs, SPI, ...next talk) should prove useful next design submission

backup

Delay Locked Loop principle

1. VCN and VCP are set to their max value (1.2 & 0 resp.).
 - ✓ The propagation delay in the DLL is then the smallest \rightarrow 11ns.
2. The delay is increased until it reaches the delay of one clock cycle.
3. The phase comparator locks then the delay of the delay line at one clock cycle

